


Experiment 2

Aim: To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.

Tool Used: LTSPICE

Theory


VIL	Input Low Voltage
	Any voltage between 0 and VIL treated as Logic Zero
VOH	Output High Voltage
	Any output voltage level between VOH and VDD treated as Logic One
VIH	Input High Voltage
	Any Input voltage level between VIH and VDD will be treated as Logic One
VOL	Output Low Voltage
	Any output voltage level between Zero and VOL treated as Logic Zero

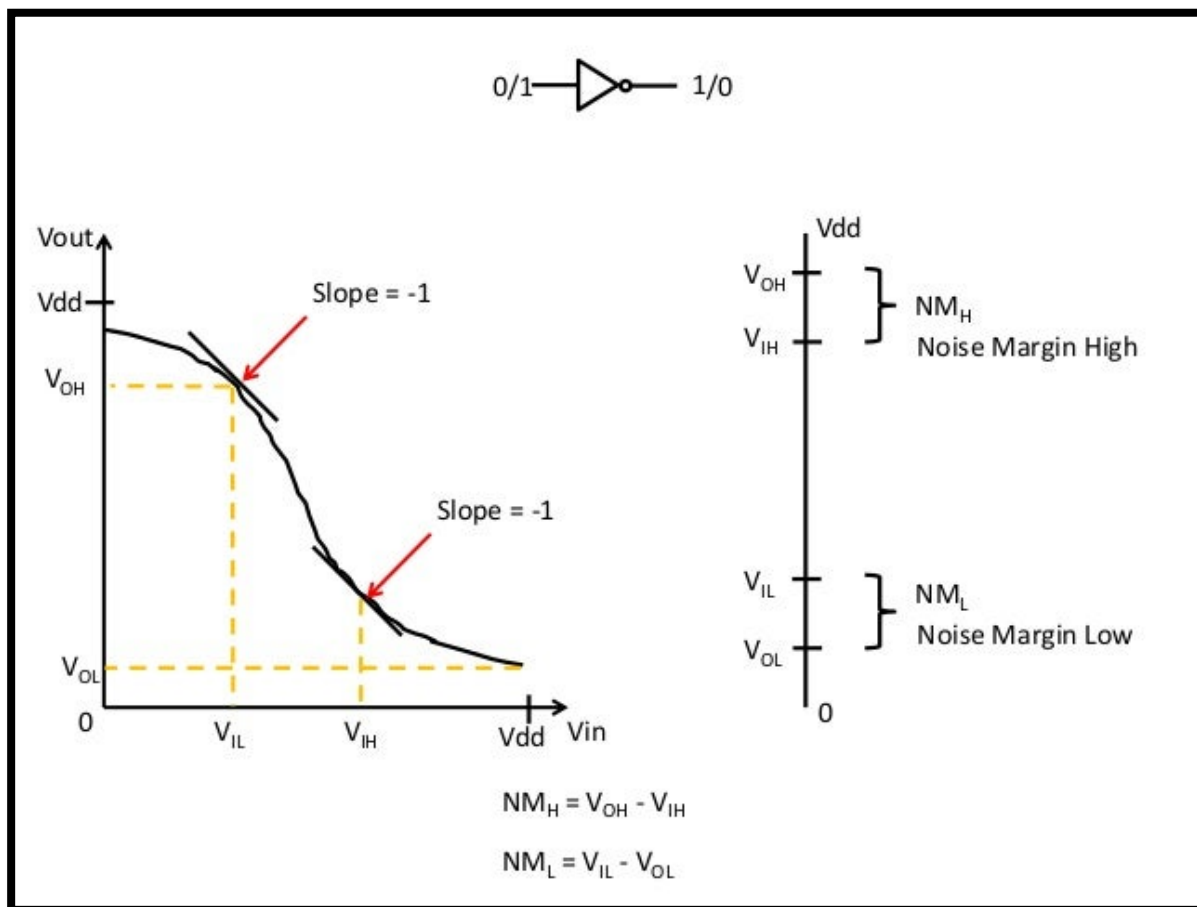

Switching Threshold: A point at which $V_{in} = V_{out}$ at this point PMOS and NMOS both are in saturation state both transistors are on. High chances of leakage current flow.

Simulation

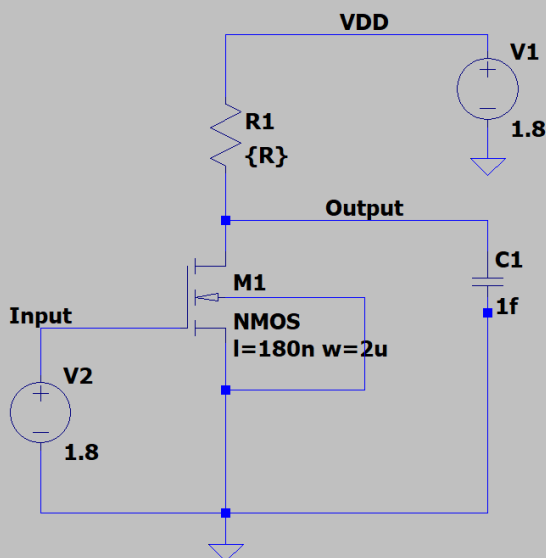Aim To perform the parametric sweep analysis on resistive load inverter to plot the VTC Curve for different values of the load resistance and calculate the various critical parameters of the VTC curve for each case.
DC Sweep Analysis to Plot VTC (Vout Vs Vin)



```
.dc V2 0 1.8 0.01
```

V2=Input, Start Value=0v, Stop Value=1.8v and Step Size =0.01v


```
.step param R list 10k 50k 100k
```

```
.meas Vth WHEN V(Input)-V(Output)=0
```

Measurement: vth

step	R	v(input)-v(output)=0
1	10K	0.9
2	50K	0.486518
3	100K	0.36

Roll Number = RS24EC01

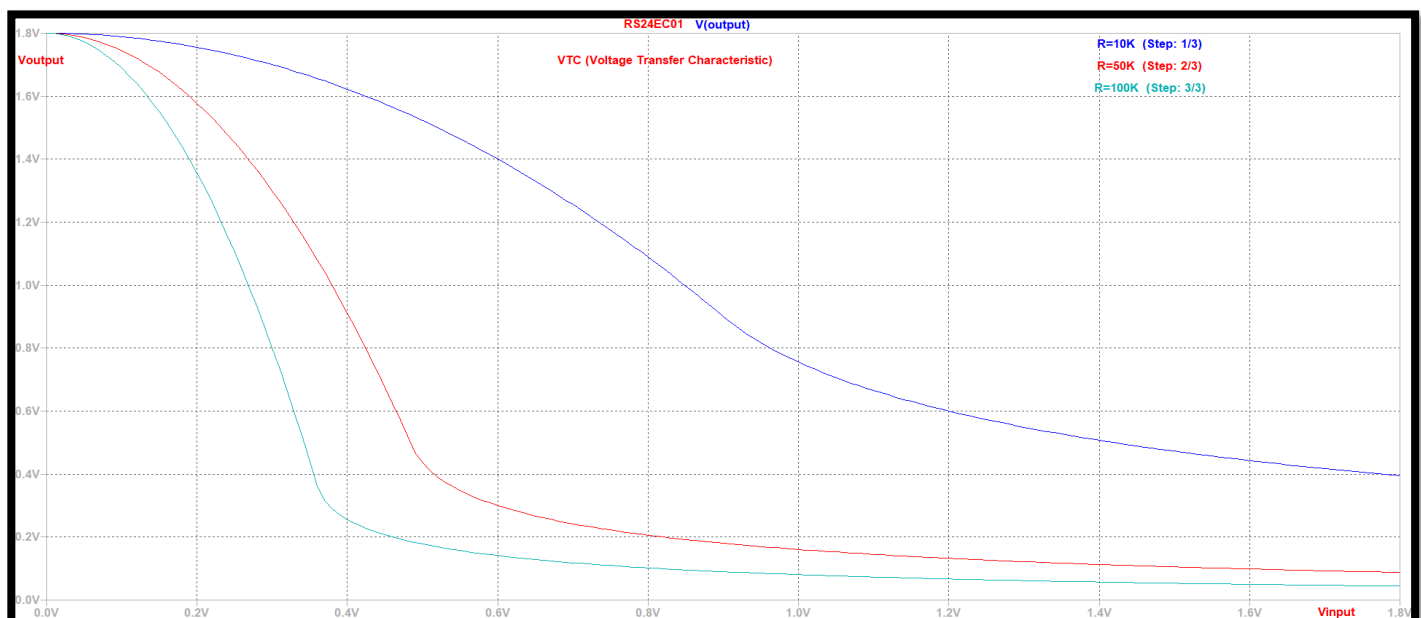


Aim : To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.



DC SWEEP Analysis to Plot VTC (Vout Vs Vin)

Simulation Commands:

```
.dc V2 0 1.8 0.01
V2=Input, Start Value=0v,Stop Value=1.8v and Step Size =0.01v
.step param R list 10k 50k 100k
```

Roll Number = RS24EC01

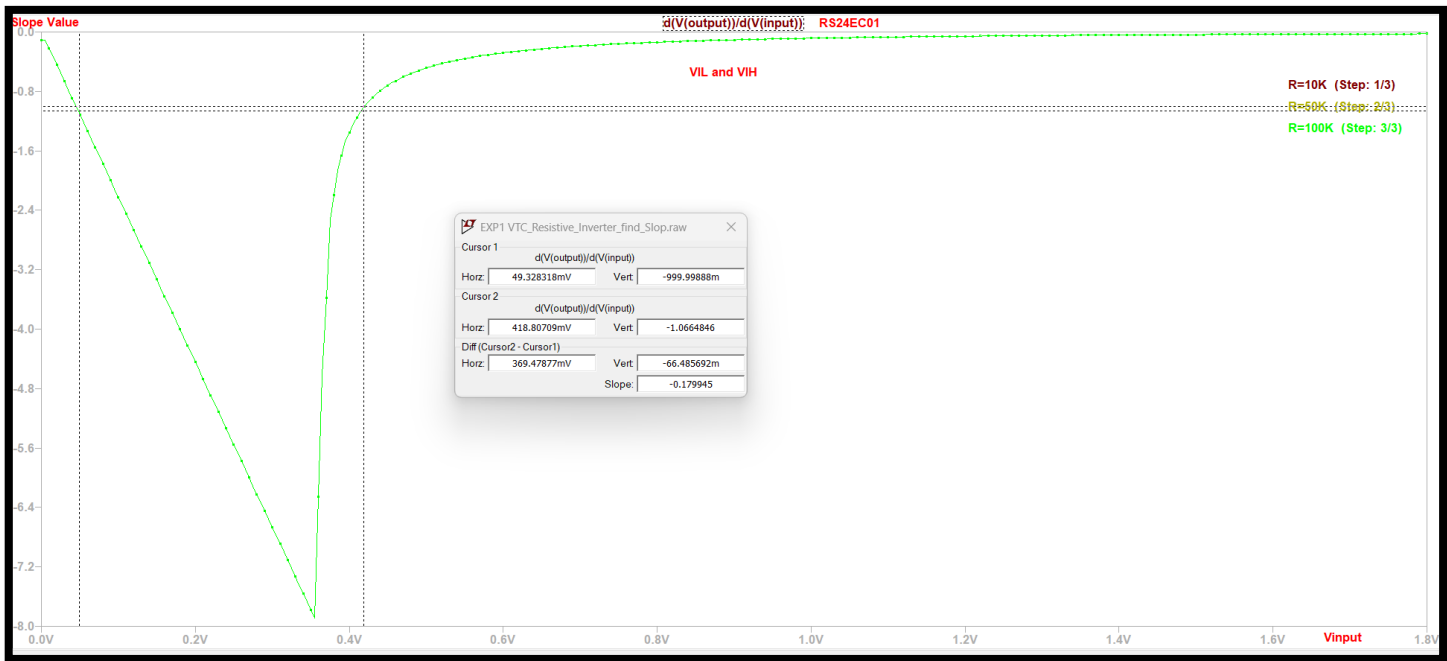


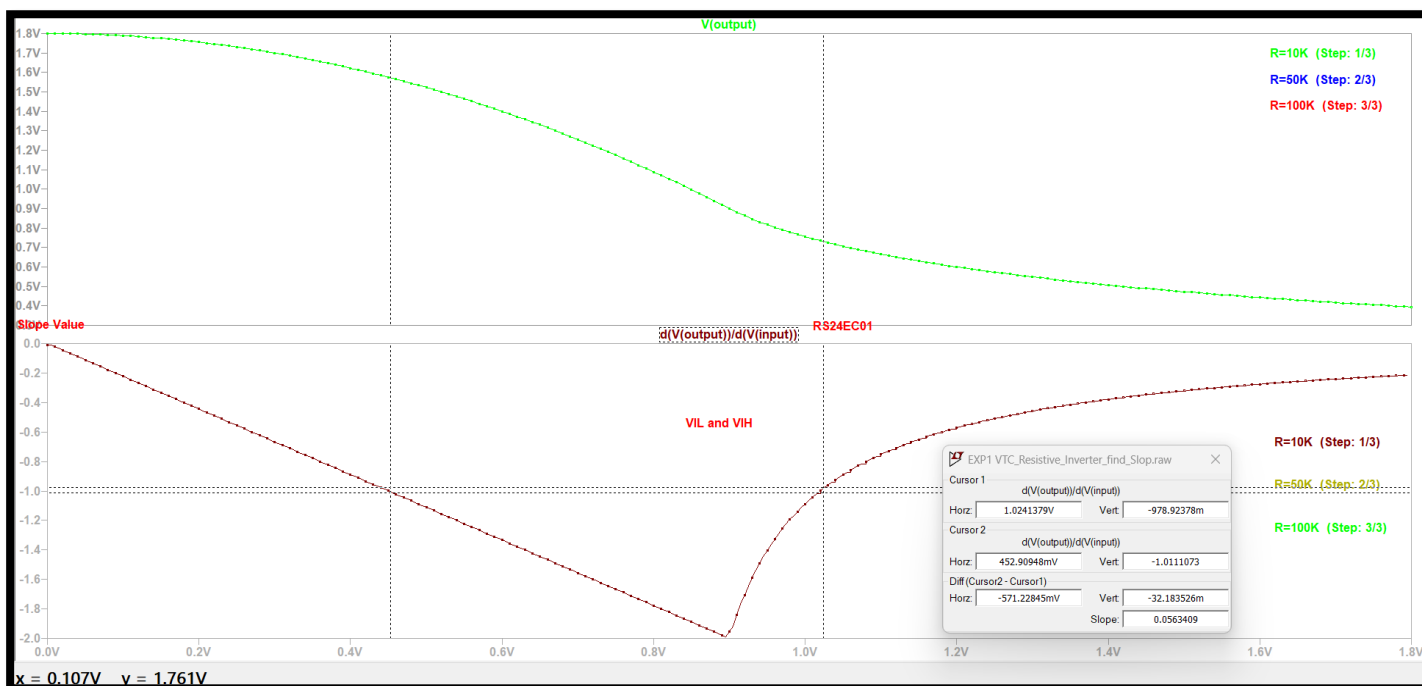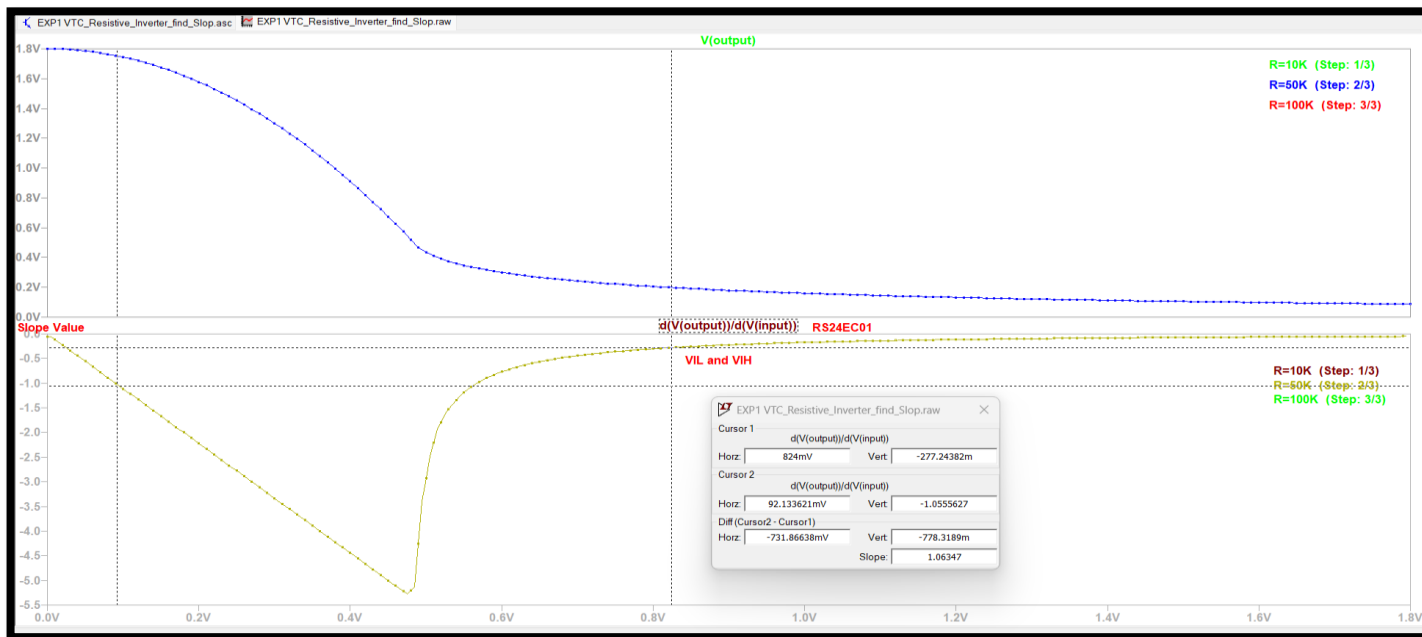

Aim : To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.

Transient Analysis

Drain Current

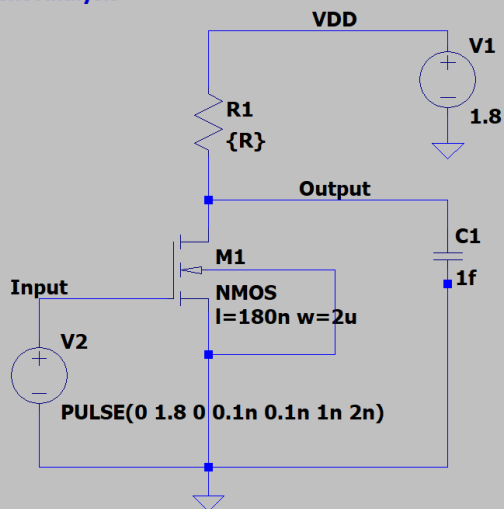




.tran 0 5n 0.01n 0.01n


Stop time =5n , Time for Saving data =0.01n ,Step Size=0.01n

.step param R list 10k 50k 100k

Roll Number = RS24EC01

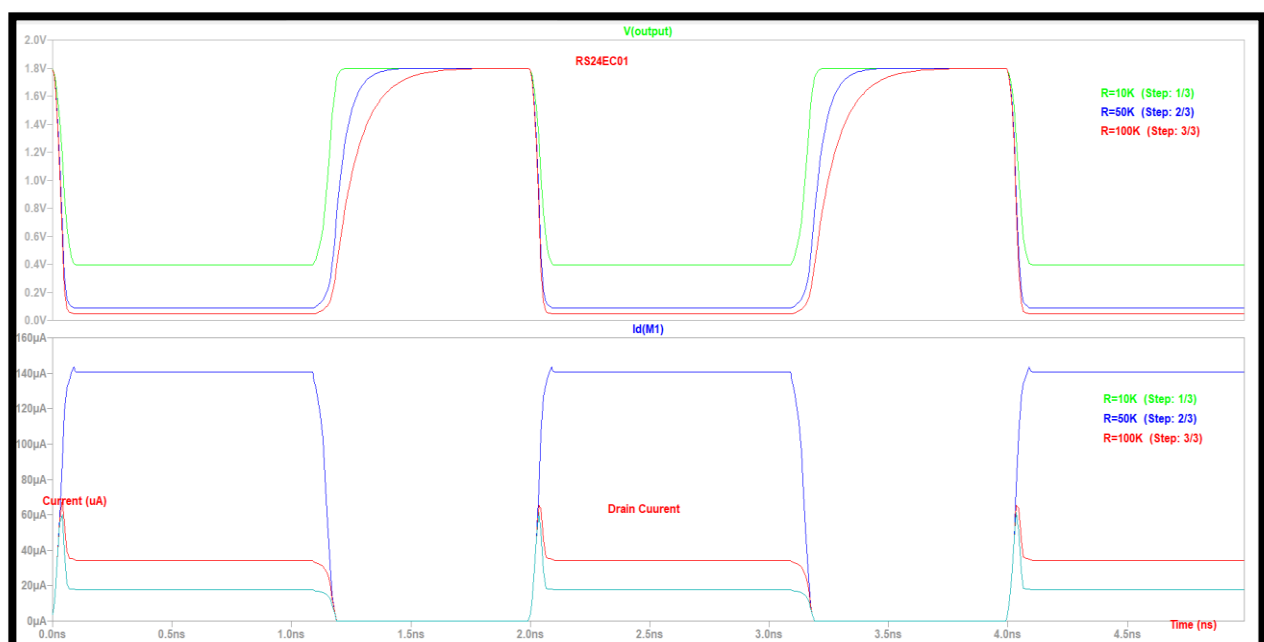


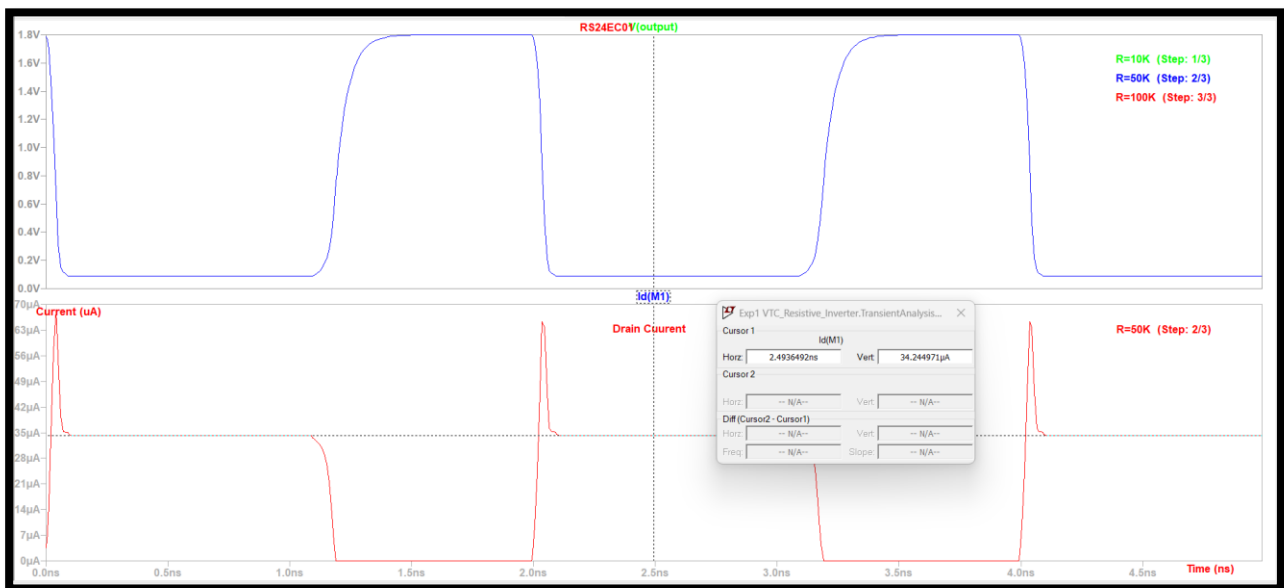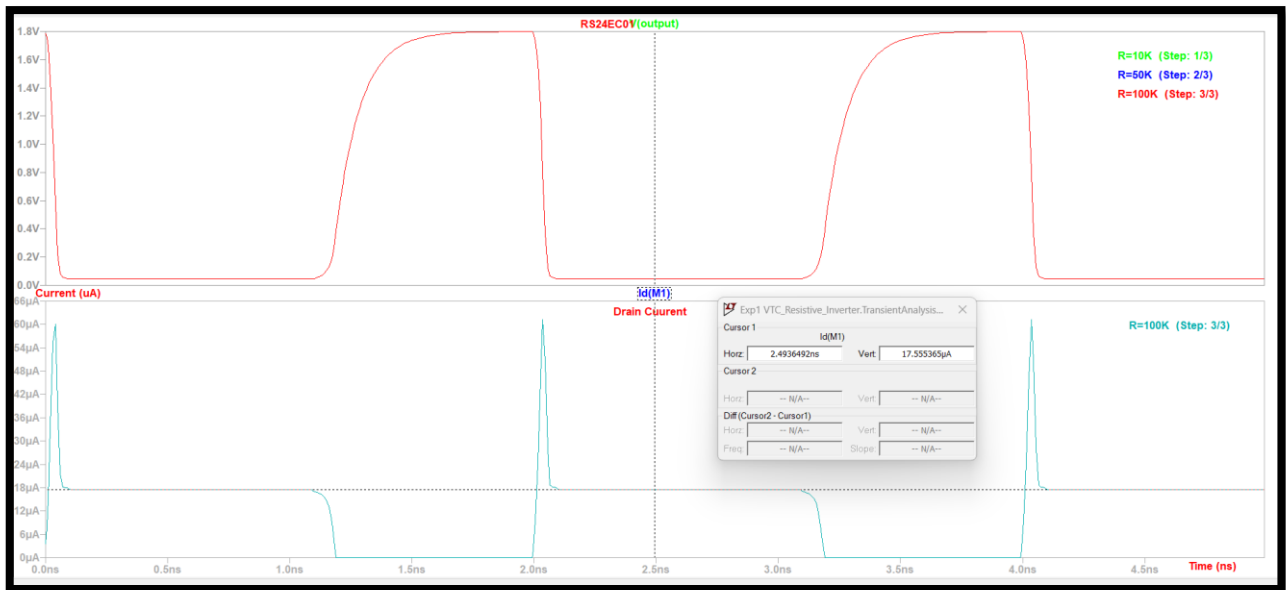

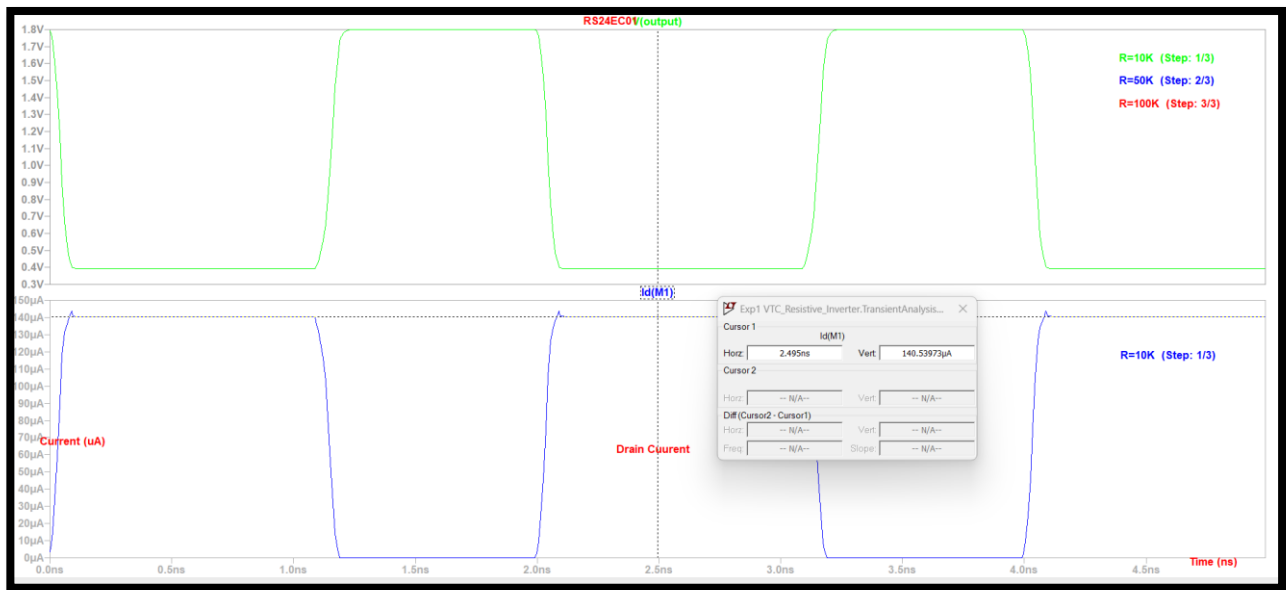

Aim : To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.

Operating Points

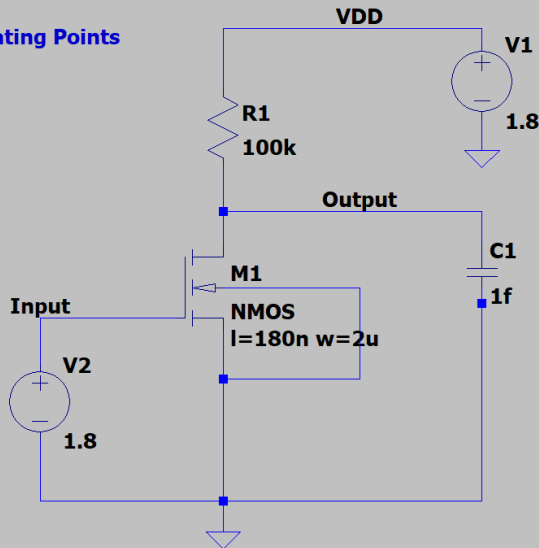

```
.op
;step param R list 10k 50k 100k
```


--- Operating Point ---

V(vdd):	1.8	voltage
V(output):	0.0444376	voltage
V(input):	1.8	voltage
Id(M1):	1.75556e-05	device_current
Ig(M1):	0	device_current
Ib(M1):	-5.26435e-14	device_current
Is(M1):	-1.75556e-05	device_current
I(C1):	4.44376e-29	device_current
I(R1):	1.75556e-05	device_current
I(V1):	-1.75556e-05	device_current
I(V2):	0	device_current

Roll Number = RS24EC01

Aim : To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.

Operating Points

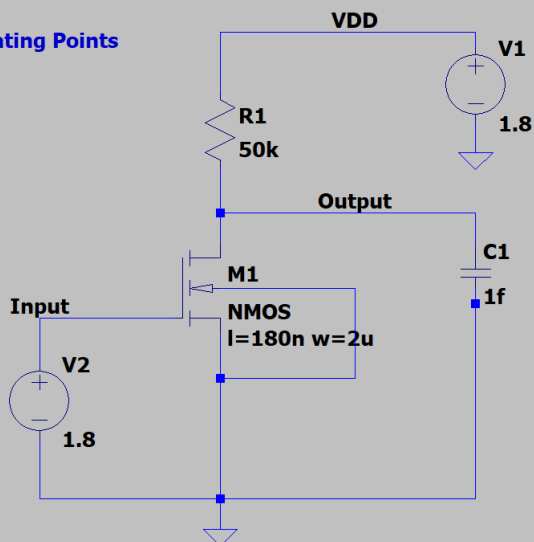

```
.op
;step param R list 10k 50k 100k
```


--- Operating Point ---

V(vdd):	1.8	voltage
V(output):	0.0877514	voltage
V(input):	1.8	voltage
Id(M1):	3.4245e-05	device_current
Ig(M1):	0	device_current
Ib(M1):	-9.74152e-14	device_current
Is(M1):	-3.4245e-05	device_current
I(C1):	8.77514e-29	device_current
I(R1):	3.4245e-05	device_current
I(V1):	-3.4245e-05	device_current
I(V2):	0	device_current

Roll Number = RS24EC01

Aim : To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.

Operating Points

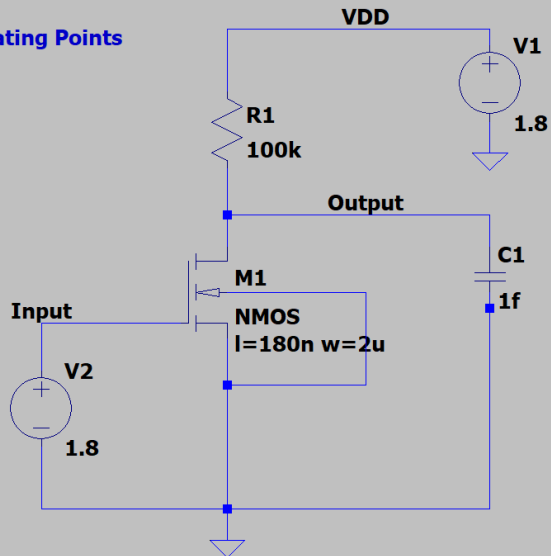

```
.op
;step param R list 10k 50k 100k
```

--- Operating Point ---


```
V(vdd):      1.8      voltage
V(output):    0.0444376 voltage
V(input):     1.8      voltage
Id(M1):       1.75556e-05 device_current
Ig(M1):       0        device_current
Ib(M1):       -5.26435e-14 device_current
Is(M1):       -1.75556e-05 device_current
I(C1):        4.44376e-29 device_current
I(R1):        1.75556e-05 device_current
I(V1):        -1.75556e-05 device_current
I(V2):        0        device_current
```

Roll Number = RS24EC01

Aim : To perform the parametric sweep analysis on resistive load inverter to plot VTC Curve for different values of the load resistance and calculate the various critical parameter of VTC Curve for each case.

Operating Points

Power Calculations

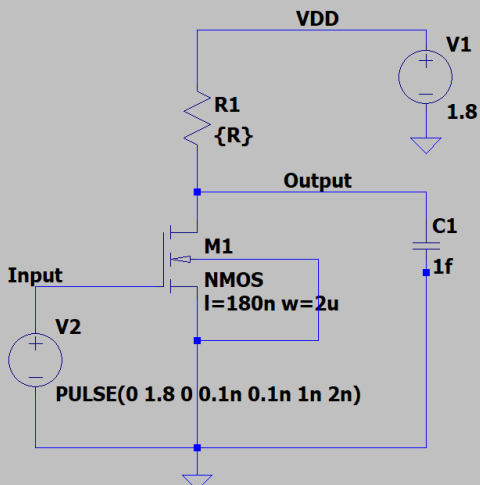

```
.tran 0 5n 0.01n 0.01n
```

Stop time =5n , Time for Saving data =0.01n ,Step Size=0.01n

```
.step param R list 10k 50k 100k
```


P=VI

AVG Power = Avg Current * VDD

P=(12.052×10⁻⁶)·1.8

P=21.69μW

Roll Number = RS24EC01

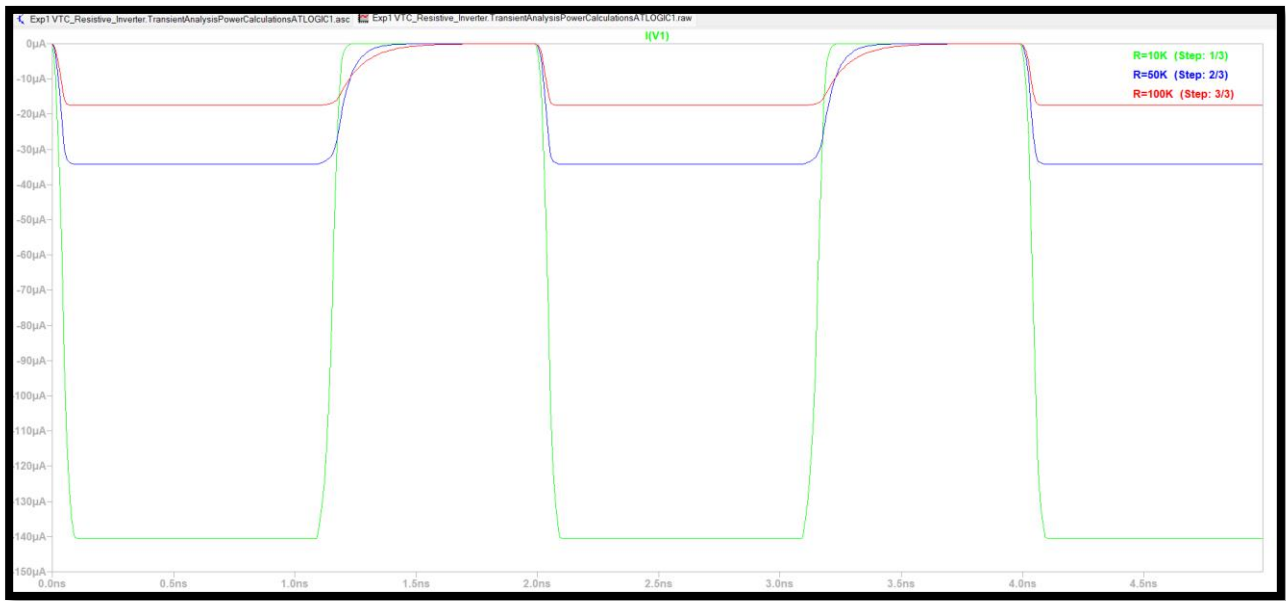

Results

Parameters	Value in mv
R=100K	
VIL	49.328318mV
VIH	418.80709mV
VOL	44.485728mV
VOH	1.8v
Vm	0.36v
Transient Analysis	
Id	17.555365μA
Power Calculation	
Avg Current	12.052μA
Avg Power	12.052μA * 1.8V
R=50K	
VIL	92.133621mV
VIH	565.40948mV
VOL	87.846385mV

VOH	1.8V
Vm	0.486v
Transient Analysis	
Id	34.244971μA
Power Calculation	
Avg Current	22.727μA
Avg Power	22.727μA*1.8V
R=10K	
VIL	452.90948mV
VIH	1.0144397V
VOL	396.88669mV
VOH	1.8V
Vm	0.9v
Transient Analysis	
Id	140.53973μA
Power Calculation	
Avg Current	89.23μA
Avg Power	89.23μA*1.8V