

Experiment 1

Aim: To Perform DC and Transient Analysis of Resistive Load Inverter Circuit

Or


To plot the VTC Curve of Resistive Load Inverter Circuit

Tool Used: LTSPICE

Theory:

Theory

| | |
|-----|--------------------------------------------------------------------------|
| VIL | Input Low Voltage |
| | Any voltage between 0 and VIL treated as Logic Zero |
| VOH | Output High Voltage |
| | Any output voltage level between VOH and VDD treated as Logic One |
| VIH | Input High Voltage |
| | Any Input voltage level between VIH and VDD will be treated as Logic One |
| VOL | Output Low Voltage |
| | Any output voltage level between Zero and VOL treated as Logic Zero |

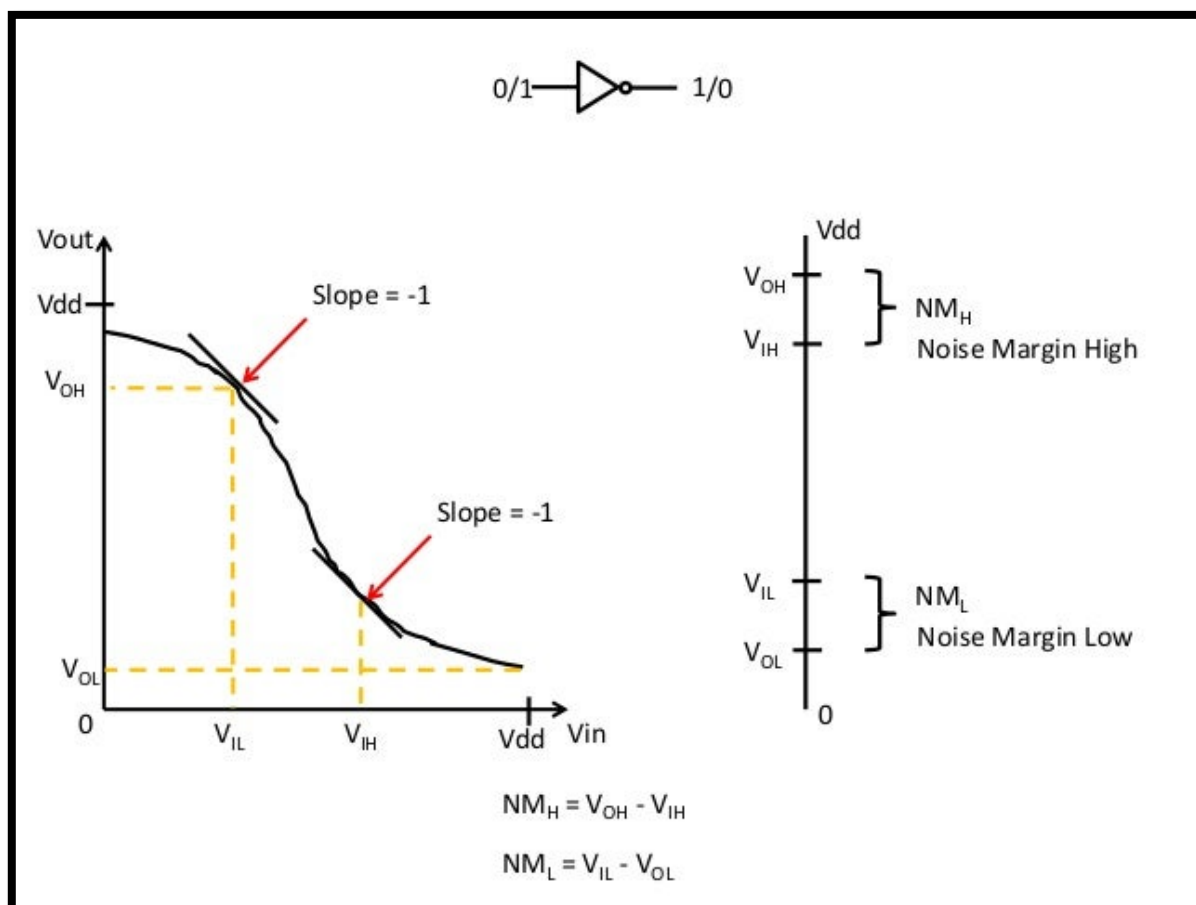


Switching Threshold: A point at which $V_{in} = V_{out}$ at this point PMOS and NMOS both are in saturation state both transistors are on. High chances of leakage current flow.

Simulation

Aim Perform the DC SWEEP Analysis and Transient Analysis of Resistive Load Inverter

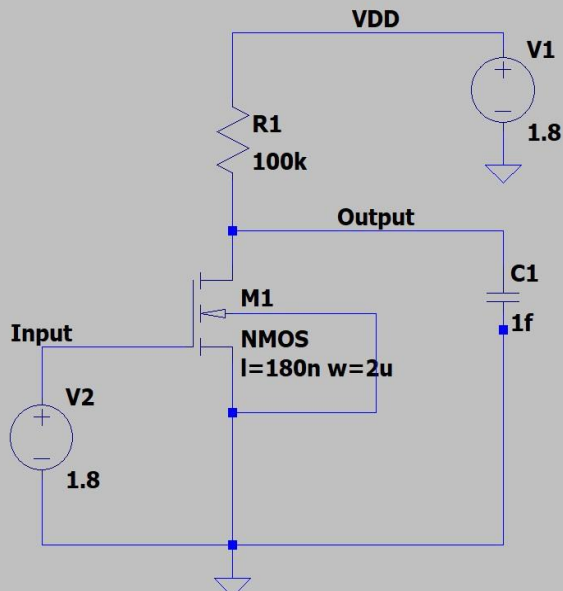
Part1 : DC SWEEP Analysis to Plot VTC (Vout Vs Vin)





.dc V2 0 1.8 0.01


V2=Input, Start Value=0v, Stop Value=1.8v and Step Size =0.01v

Roll Number = RS24EC01

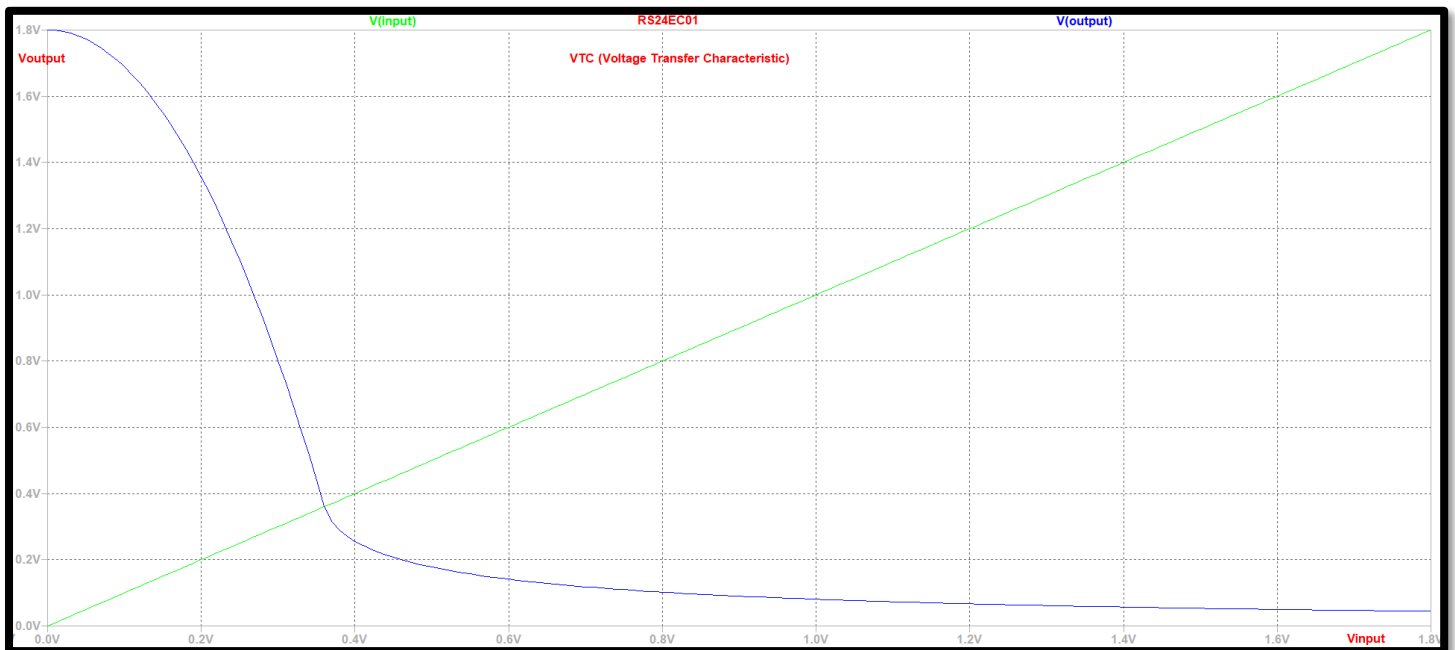

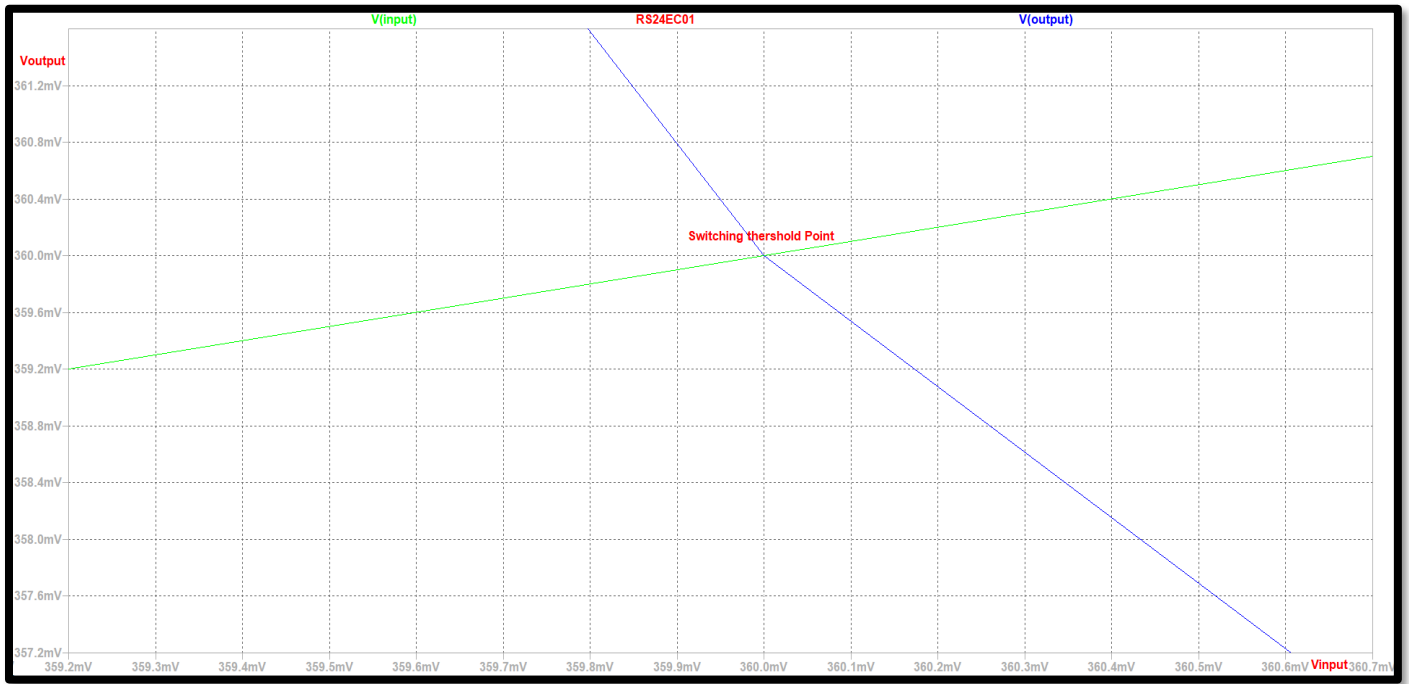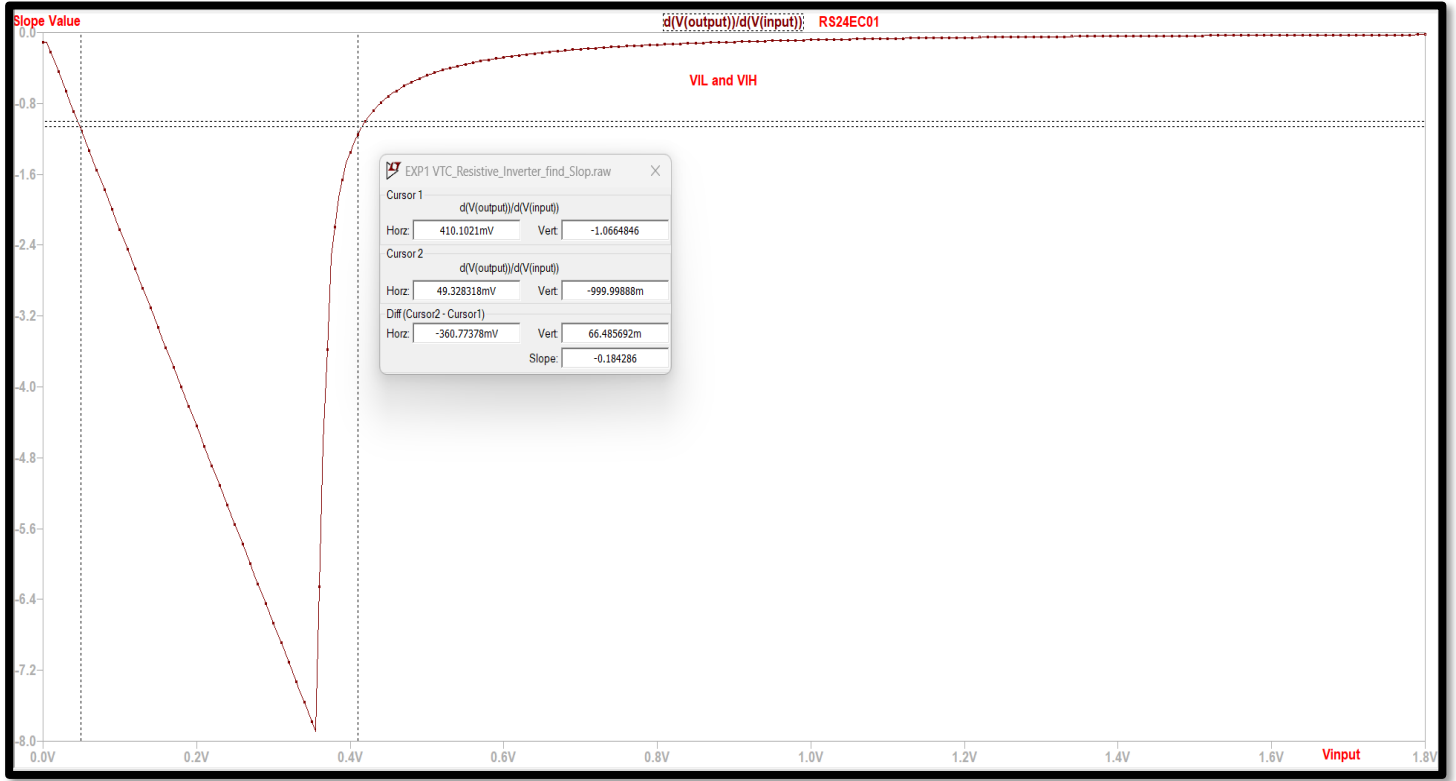

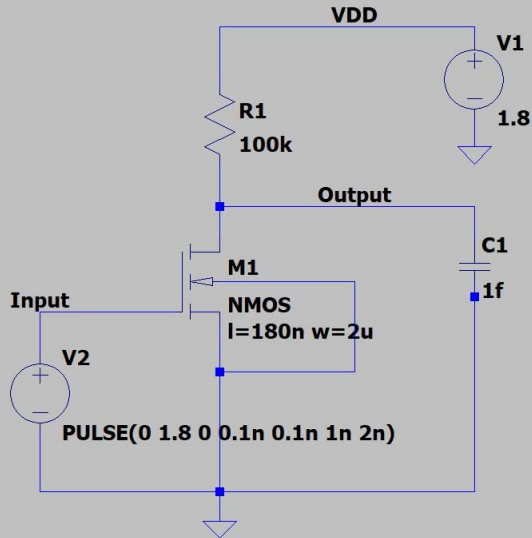
Aim Perform the DC SWEEP Analysis and Transient Analysis of Resistive Load Inverter
Part 2 : Transient Analysis




.tran 0 5n 0.01n 0.01n

Stop time =5n , Time for Saving data =0.01n ,Step Size=0.01n


Roll Number = RS24EC01

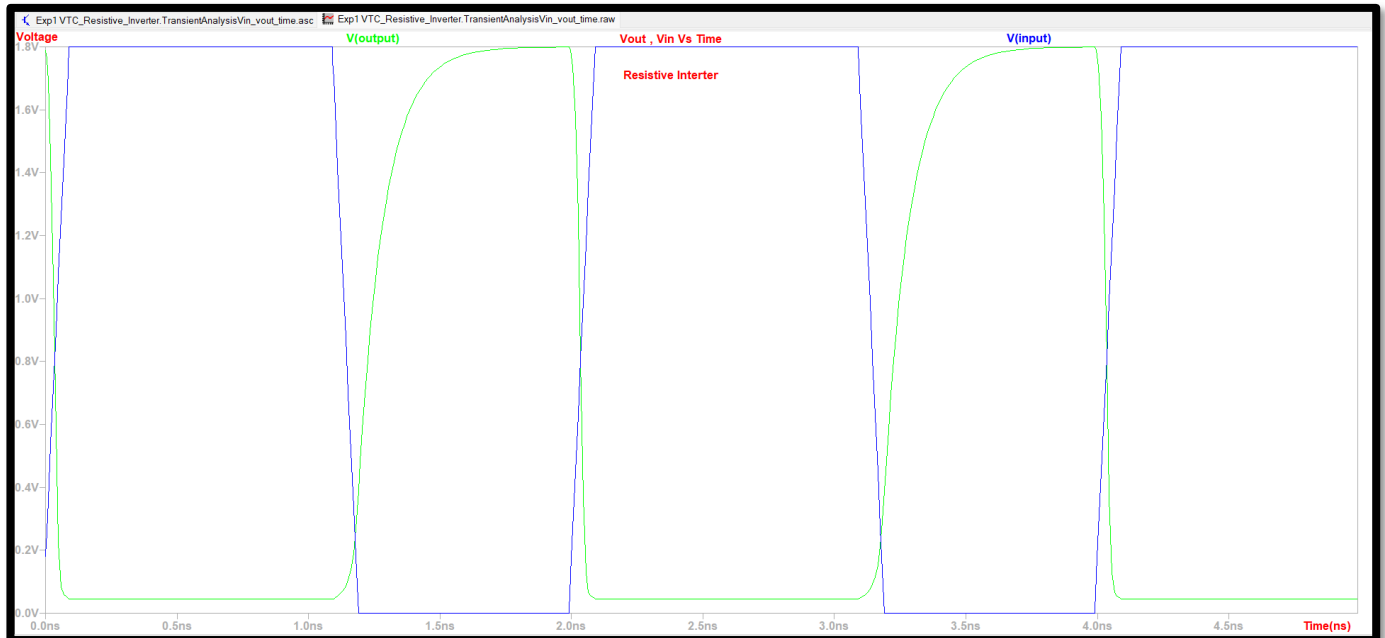

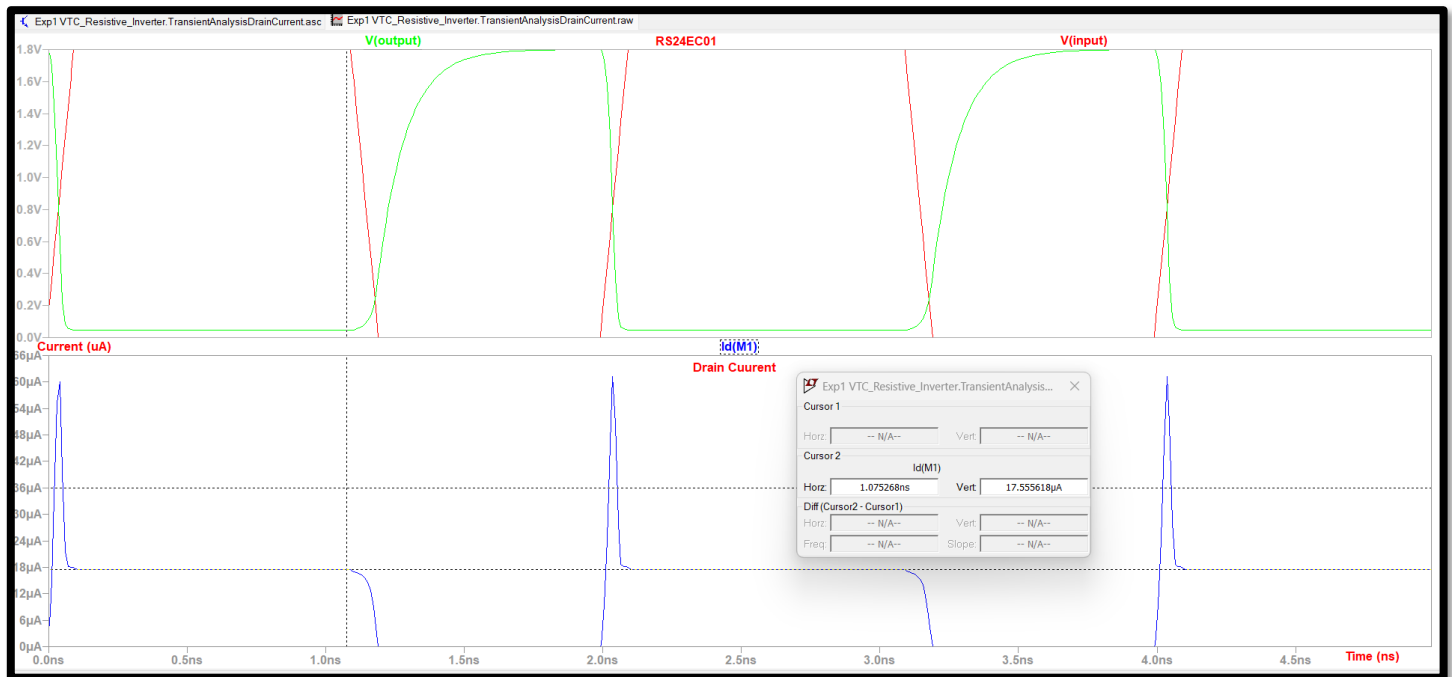

Aim Perform the DC SWEEP Analysis and Transient Analysis of Resistive Load Inverter

Part 2 : Transient Analysis

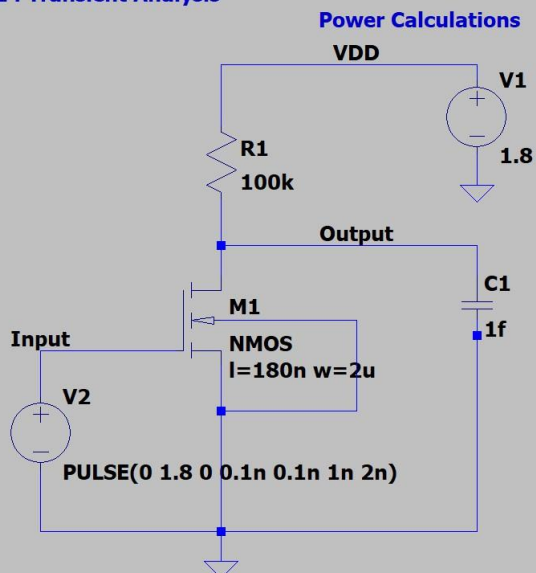

.tran 0 5n 0.01n 0.01n

Stop time =5n , Time for Saving data =0.01n ,Step Size=0.01n


$P=VI$

AVG Power = Avg Current * VDD


$P=(12.052 \times 10^{-6}) \cdot 1.8$

$P=21.69\mu W$

Roll Number = RS24EC01

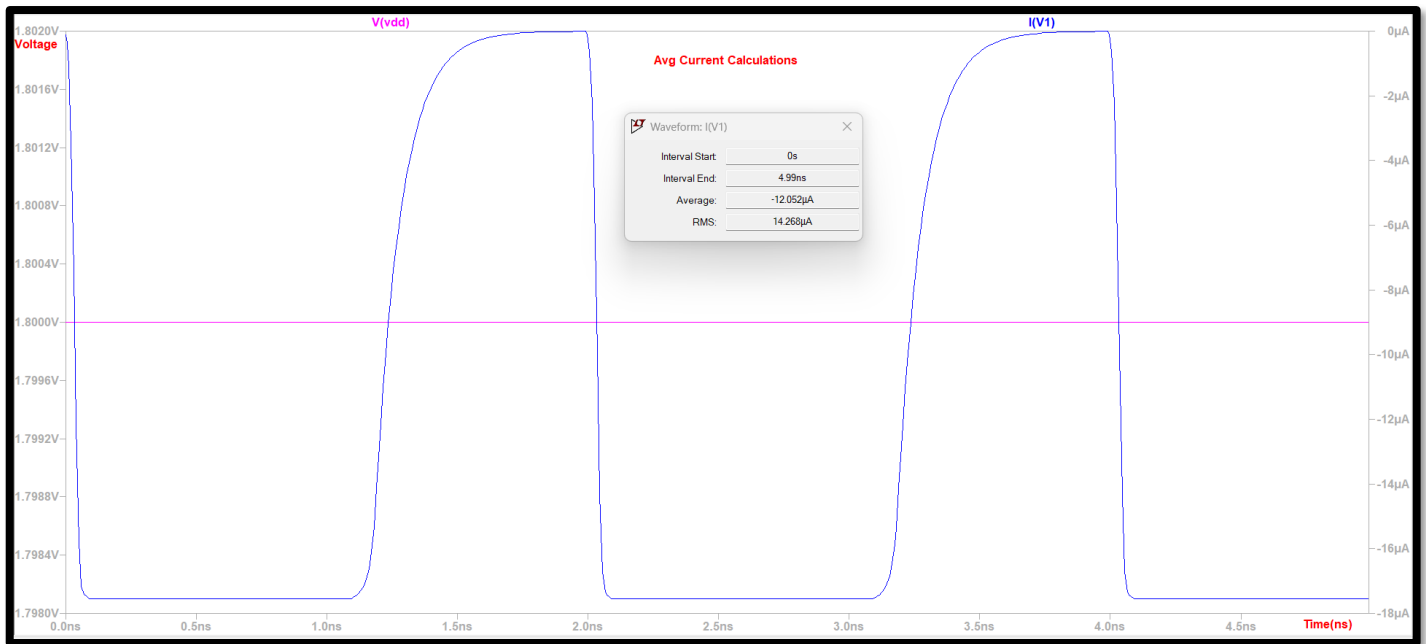

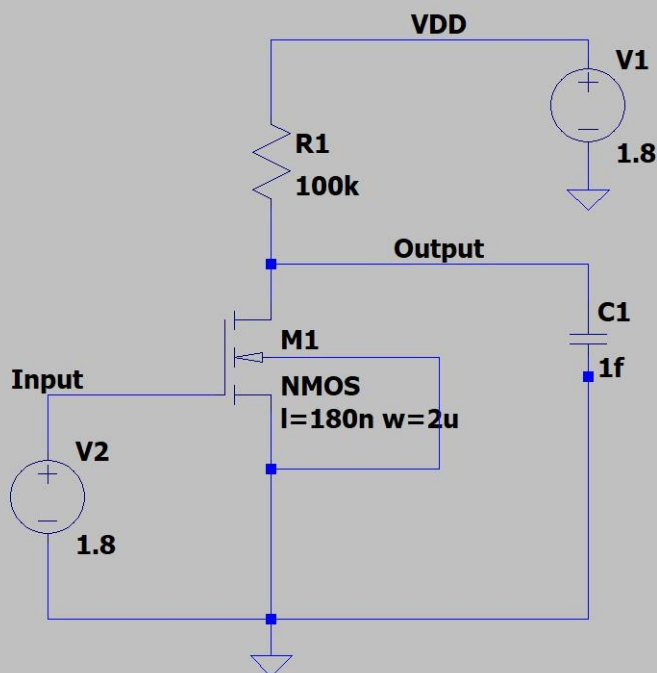Aim Perform the DC SWEEP Analysis and Transient Analysis of Resistive Load Inverter Operating Points




.op

Output
--- Operating Point ---

| | | |
|------------|--------------|----------------|
| V(vdd): | 1.8 | voltage |
| V(output): | 0.0444376 | voltage |
| V(input): | 1.8 | voltage |
| Id(M1): | 1.75556e-05 | device_current |
| Ig(M1): | 0 | device_current |
| Ib(M1): | -5.26435e-14 | device_current |
| Is(M1): | -1.75556e-05 | device_current |
| I(C1): | 4.44376e-29 | device_current |
| I(R1): | 1.75556e-05 | device_current |
| I(V1): | -1.75556e-05 | device_current |
| I(V2): | 0 | device_current |

Roll Number = RS24EC01

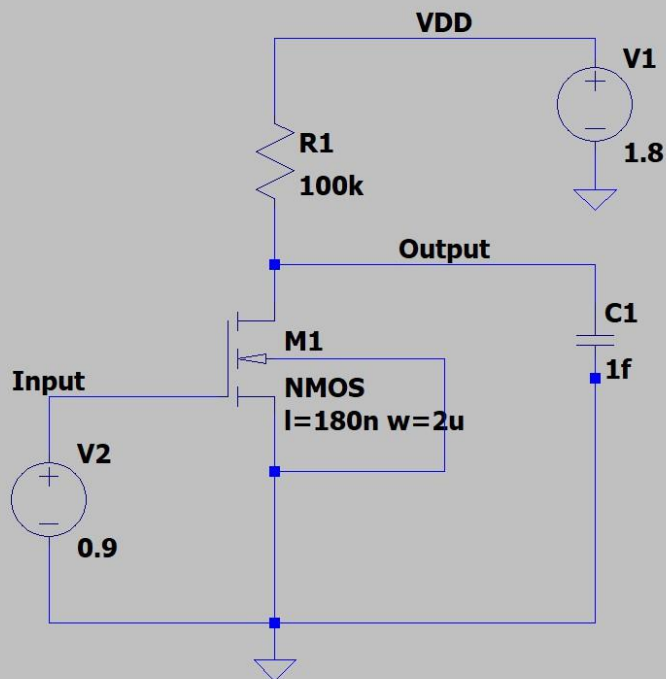Aim Perform the DC SWEEP Analysis and Transient Analysis of Resistive Load Inverter Operating Points



.op

Results
--- Operating Point ---

V(vdd): 1.8 voltage
V(output): 0.09 voltage
V(input): 0.9 voltage
Id(M1): 1.71e-05 device_current
Ig(M1): 0 device_current
Ib(M1): -9.96918e-14 device_current
Is(M1): -1.71e-05 device_current
I(C1): 9e-29 device_current
I(R1): 1.71e-05 device_current
I(V1): -1.71e-05 device_current
I(V2): 0 device_current

Roll Number = RS24EC01

Results

| Parameters | Value in mv | Value in Volt |
|---------------------------|-------------|---------------|
| VIL | 49.328318mV | 0.049328318 V |
| VIH | 410.1021mV | 0.4101021 V |
| VOL | 44.437587mV | 0.044437587 V |
| VOH | 1.8v | 1.8 V |
| Vm | 360 mV | |
| Trans Analysis | | |
| Id | 17.555365μA | |
| Power Calculations | | |
| Avg Current | 12.052μA | |
| Avg Power P= VI | 21.69μW | |